

ELEC 4700

ASSIGNMENT 4 – Circuit Modelling

Submitted By:

Jarikre Efe Jeffery

Date Submitted:

05/04/2020

Introduction:

Part 1:

By performing the first order linear fit from the previous assignment, we are able to get the value for R3 to be 10.

The differential equations that represent the network in the time domain using KCL (Summation of I=0 at the node) can be found below:

Equations:

$$\begin{aligned}V_1 &= V_{in} \\G_1(V_2 - V_1) + C \frac{d(V_2 - V_1)}{dt} + G_2 V_2 - I_L &= 0 \\V_2 - V_3 - L \frac{dI_L}{dt} &= 0 \\-I_L + G_3 V_3 &= 0 \\V_4 - \alpha I_3 &= 0 \\G_3 V_3 - I_3 &= 0 \\G_4(V_O - V_4) + G_O V_O &= 0\end{aligned}$$

Matrices:

$$\mathbf{C} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -C & C & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & -L & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \quad \mathbf{G} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -G_1 & G_1 + G_2 & -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & G_3 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -\alpha & 1 & 0 & 0 \\ 0 & 0 & 0 & G_3 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -G_4 & G_4 + G_O \end{bmatrix}$$
$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \\ I_L \\ V_3 \\ I_3 \\ V_4 \\ V_O \end{bmatrix} \quad \mathbf{F} = \begin{bmatrix} V_{in} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Equations in the frequency domain can be found below:

In the frequency domain:

Date

$$V_1 = V_{in}$$

$$G_1 (V_2 - V_1) + C j\omega (V_2 - V_1) + G_0 V_2 - I_L = 0$$

$$V_2 - V_1 - L j\omega I_L = 0$$

$$-I_L + G_3 V_3 = 0$$

$$V_4 - \alpha I_3 = 0$$

$$G_3 V_3 - I_3 = 0$$

$$G_4 (V_0 - V_4) + G_0 V_0 = 0$$

Programming section:

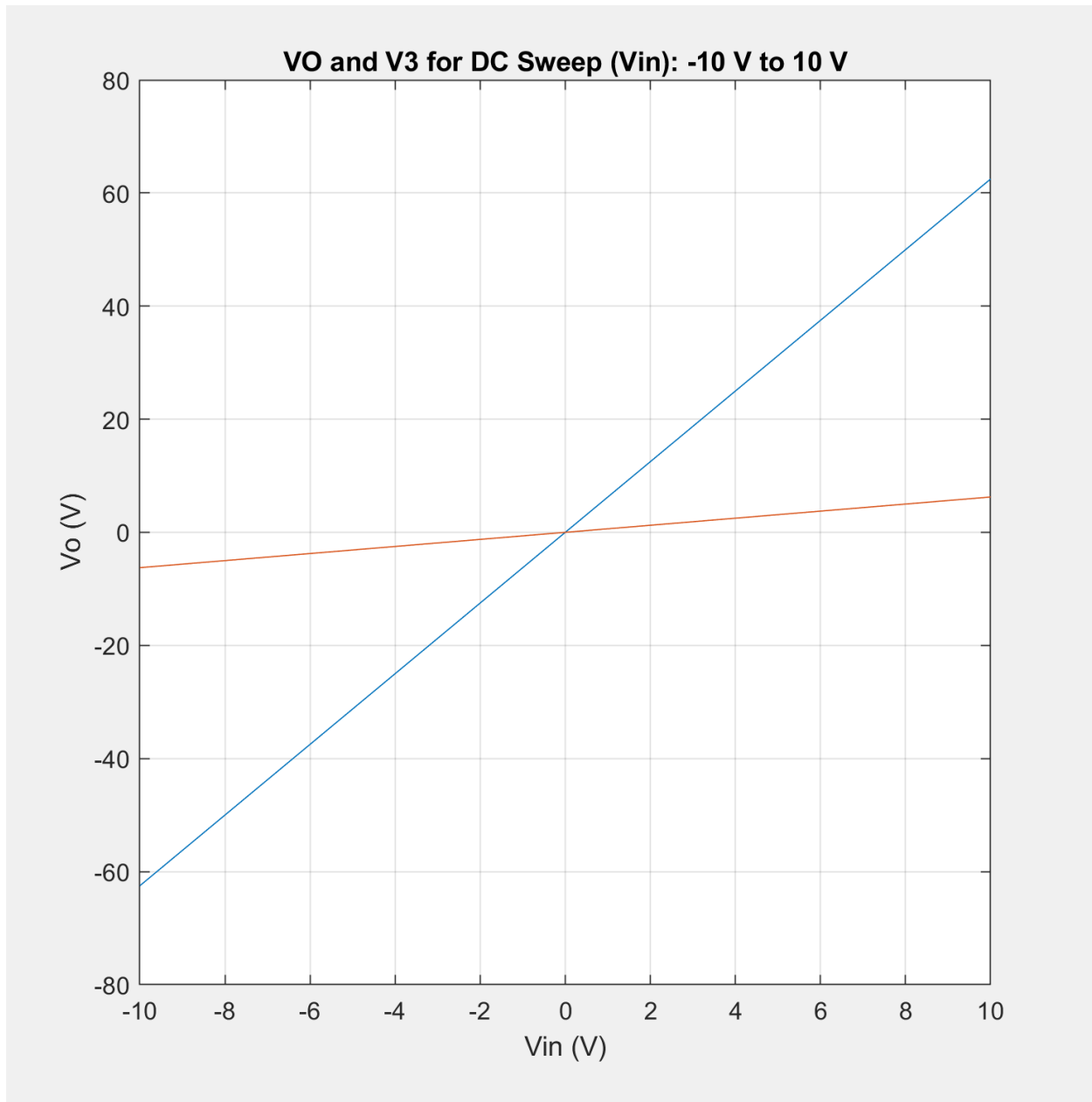


Figure 1: DC Sweep of the input voltage

 


Figure 2: Ac plot of Vo as a fuction of w

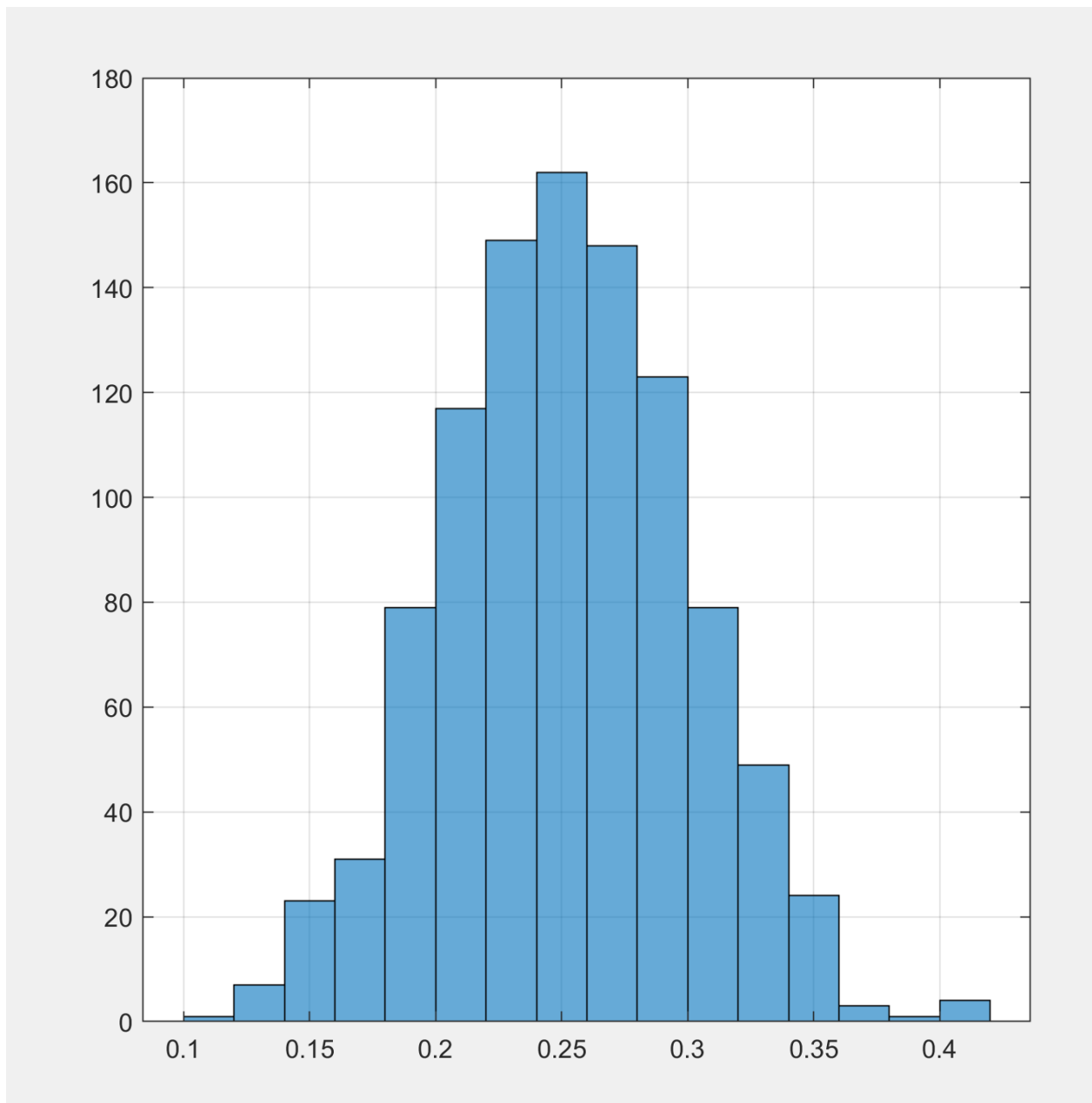


Figure 3: Histogram plot 1

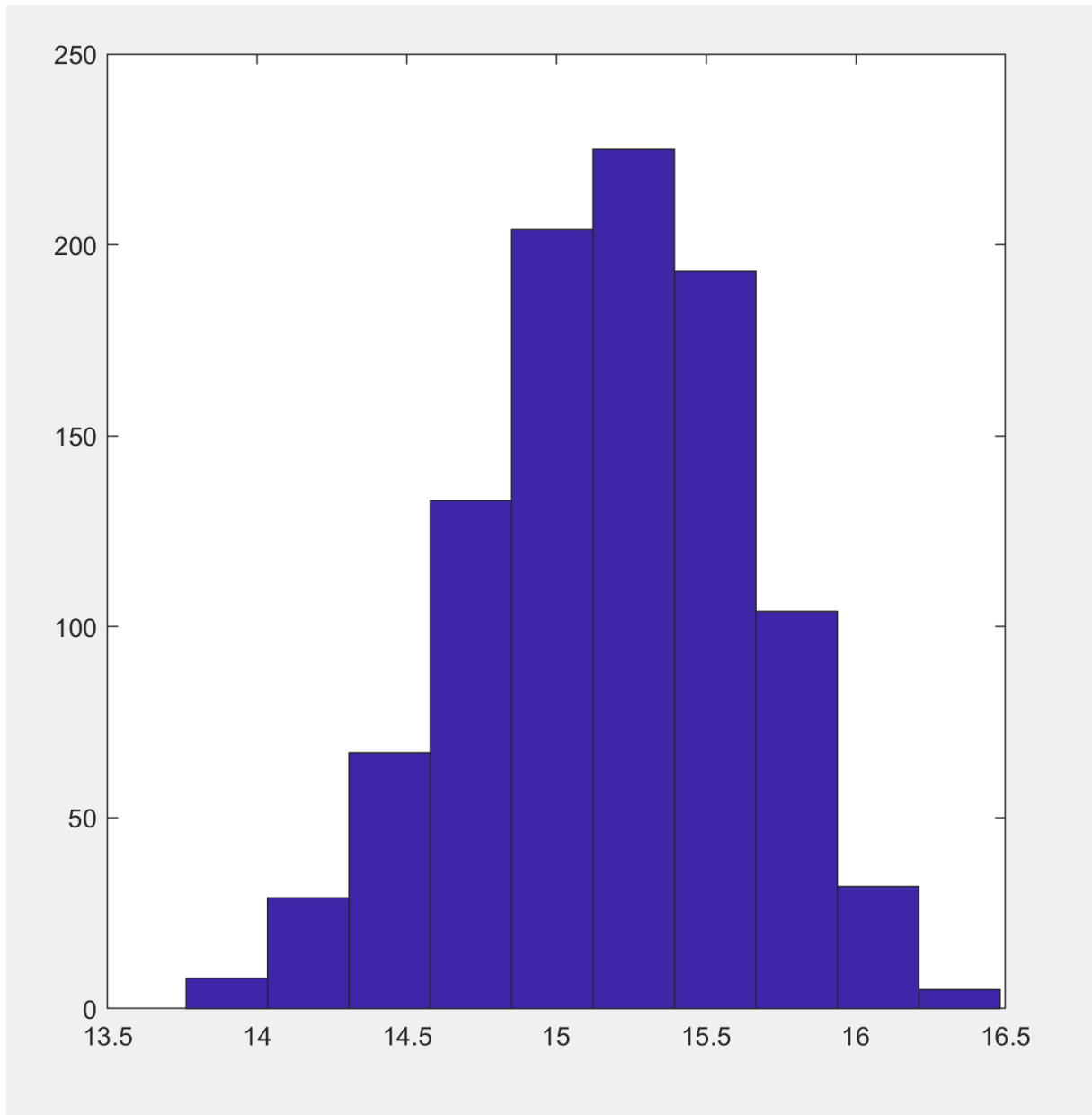


Figure 4: Histogram plot 2

Transient Simulation:

The circuit can be simulated in the time domain by solving the equation of $CdV/dt + GV = F$

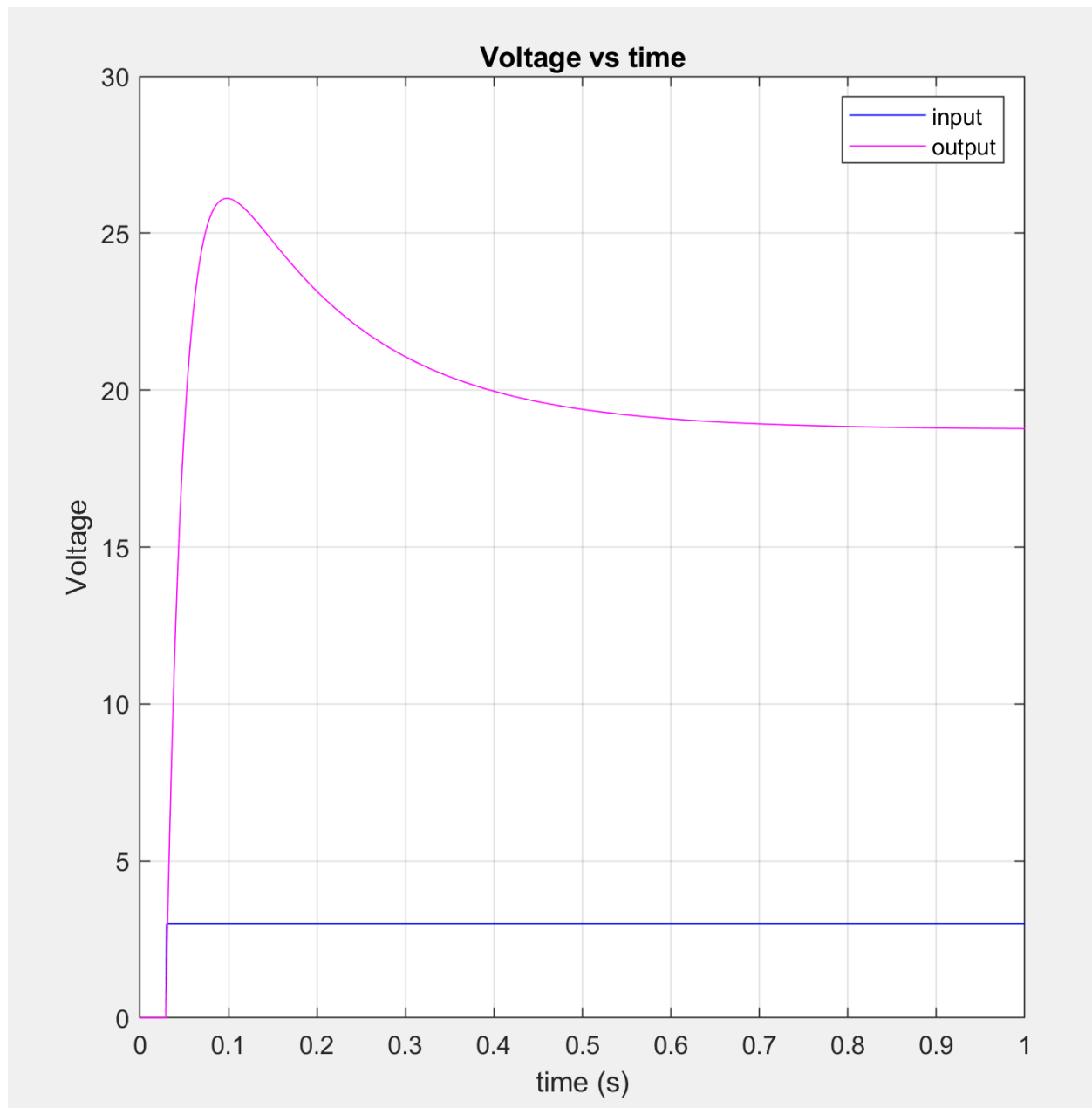


Figure 5: Plot of the voltage vs time

- a.) By inspection the circuit is a low pass filter
- b.) We should expect the frequency response to cut off high frequencies and allow only the low frequencies to go through.
- d.) Part v: As the time step is increased the accuracy of the simulation is decreased.

 


Figure 6: voltage vs time input and output sinusoid

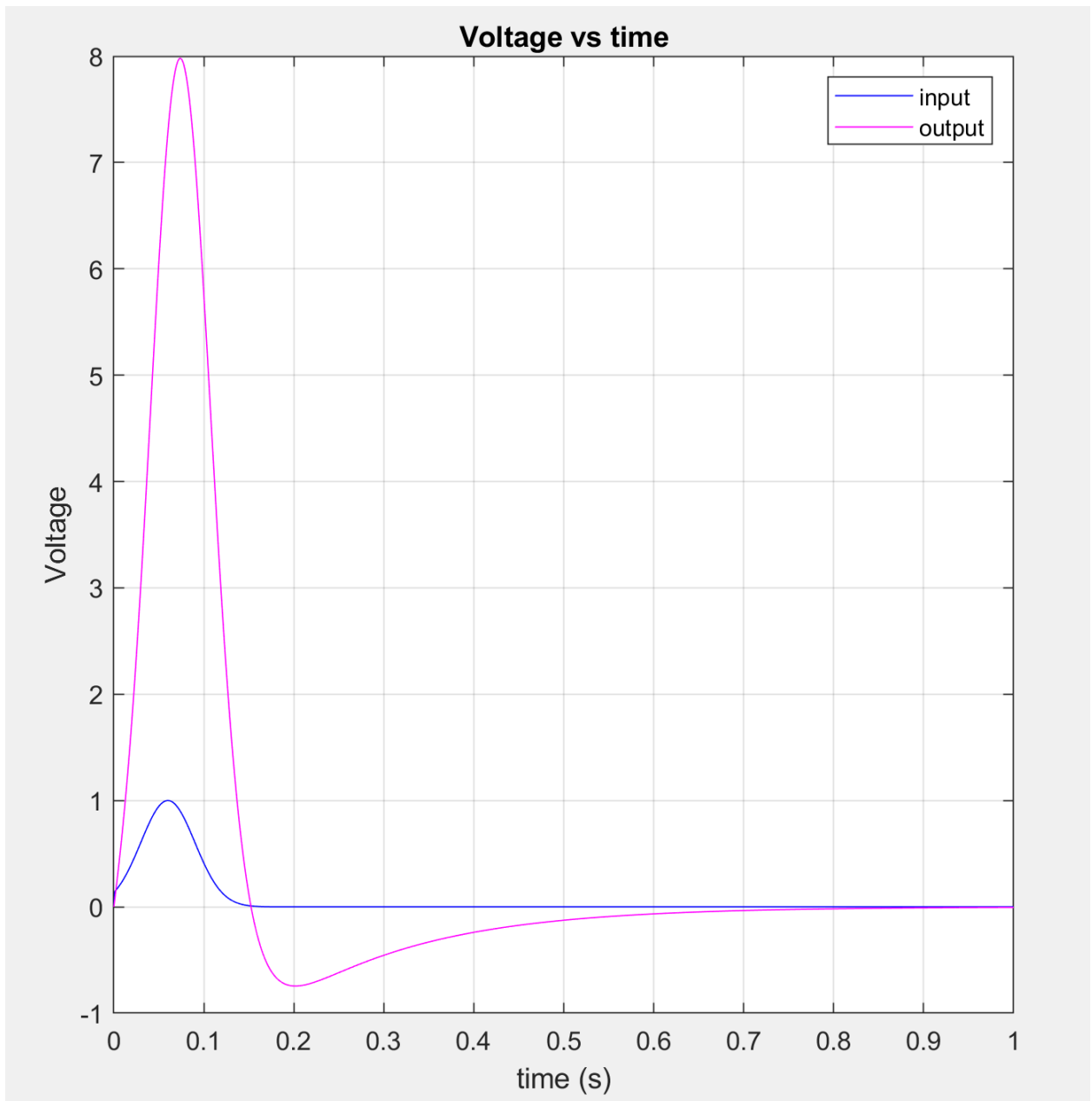


Figure 7: voltage vs time with input and output

 


Figure 8: frequency content step input

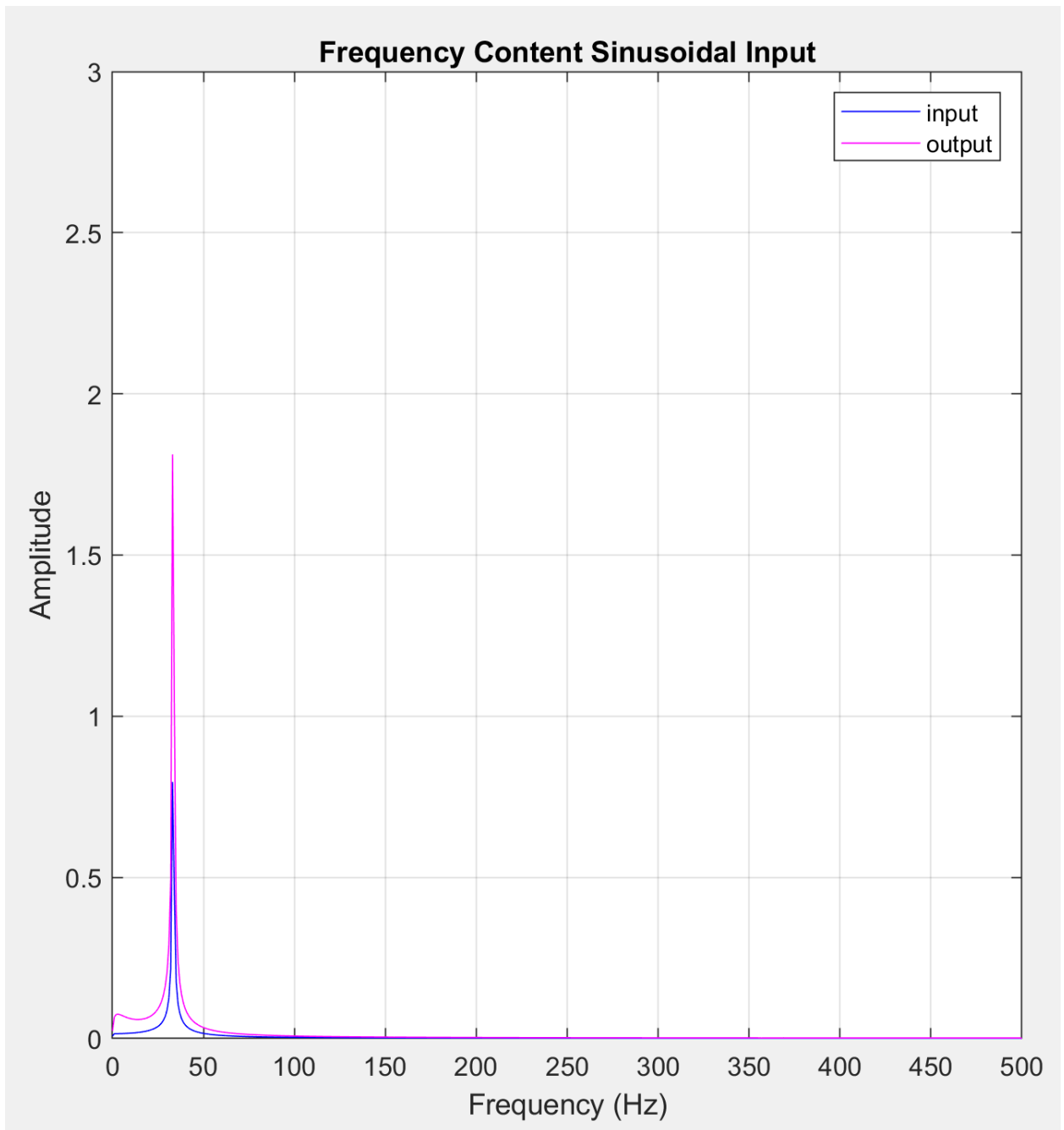


Figure 9: Frequency content sinuisoidal input

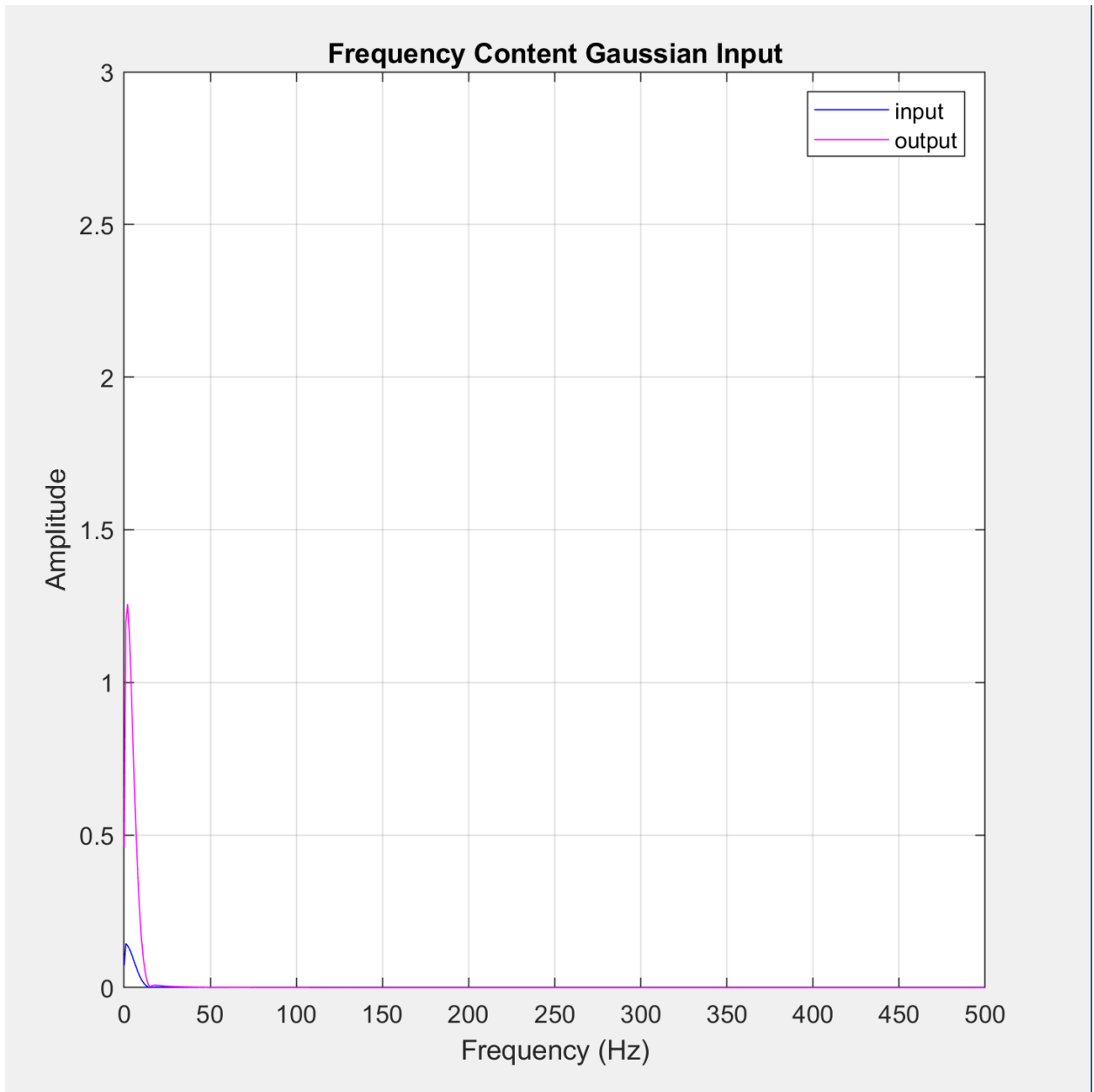


Figure 10: Frequency content Gaussian input

C matrix:

C1 =

0.2500	-0.2500	0	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0	0
0	0	0.0000	0	0	0	0	0
0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0
0	0	0	0	0	-0.2000	0	0
0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0

Note That Cn1 = 0.00001

$C1(1,:) = [C \quad -C \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0];$

$C1(2,:) = [-C \quad C \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0];$

$C1(3,:) = [0 \quad 0 \quad cn1 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0];$

$C1(4,:) = [0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0];$

$C1(5,:) = [0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0];$

$C1(6,:) = [0 \quad 0 \quad 0 \quad 0 \quad 0 \quad -L \quad 0 \quad 0];$

$C1(7,:) = [0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0];$

$C1(8,:) = [0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0];$

Varying Cn:

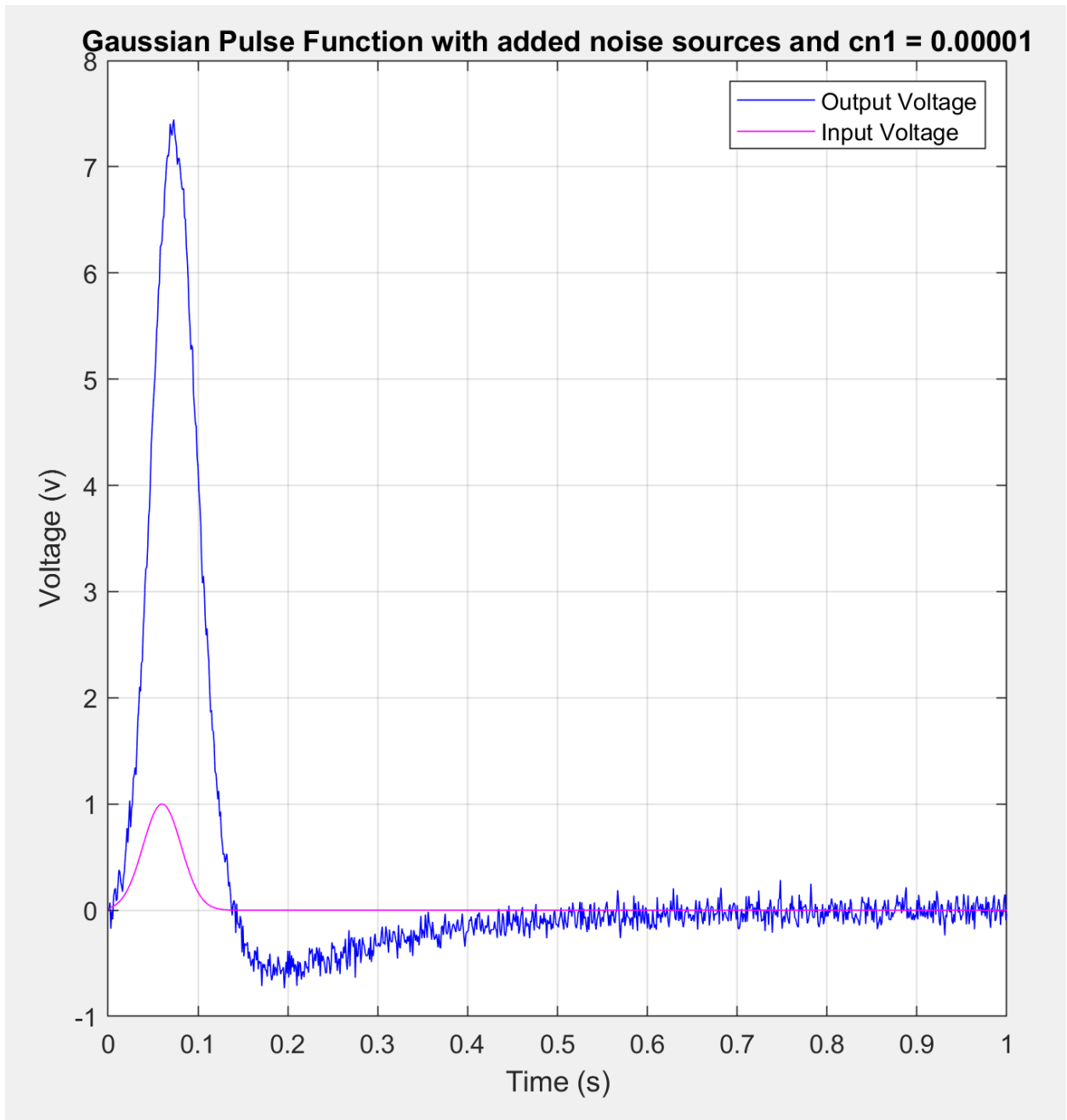


Figure 11: Gaussian Pulse function with added noise sources and $cn1 = 0.00001$

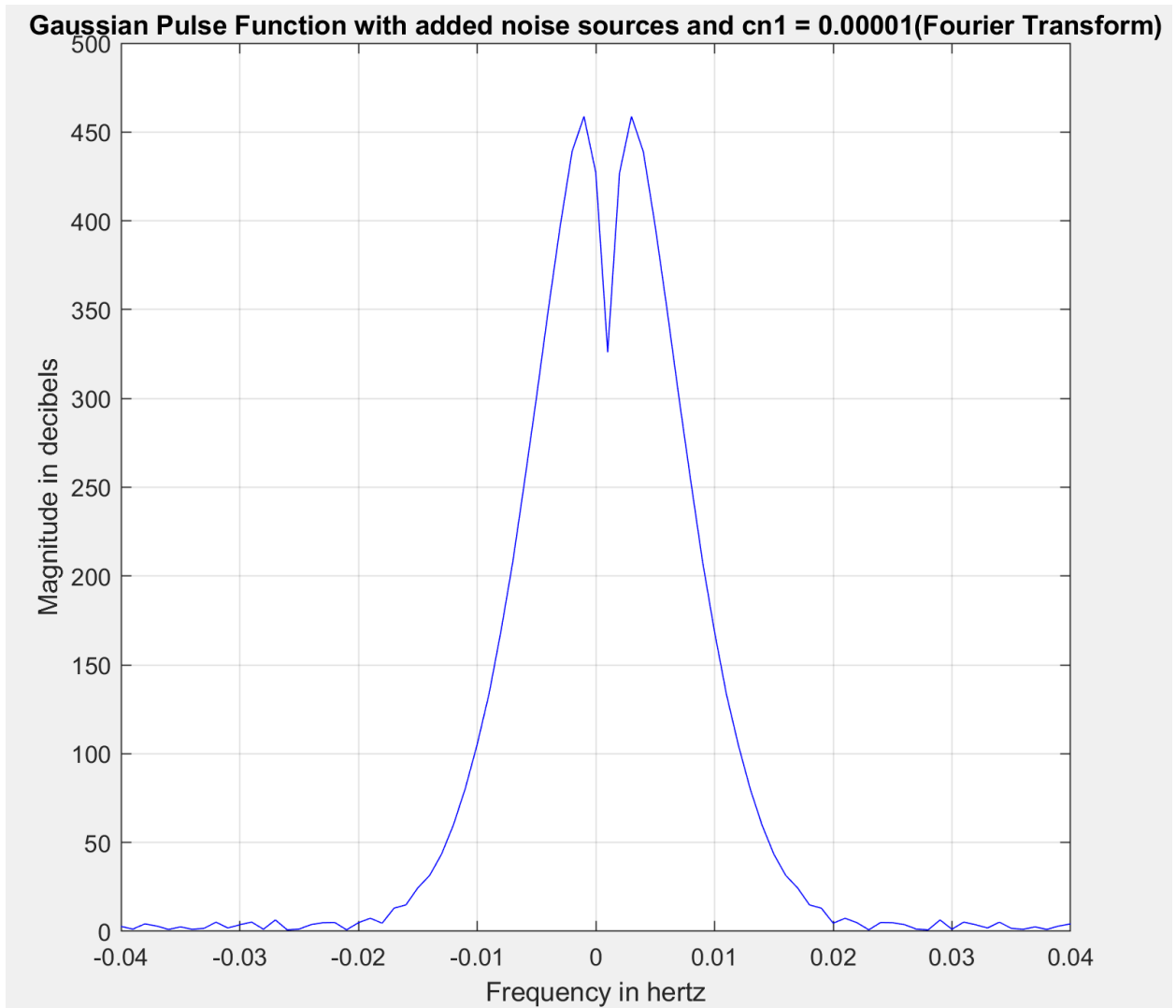


Figure 12: Gaussian Pulse function with added noise sources and $cn1=0.00001$
fourier transform

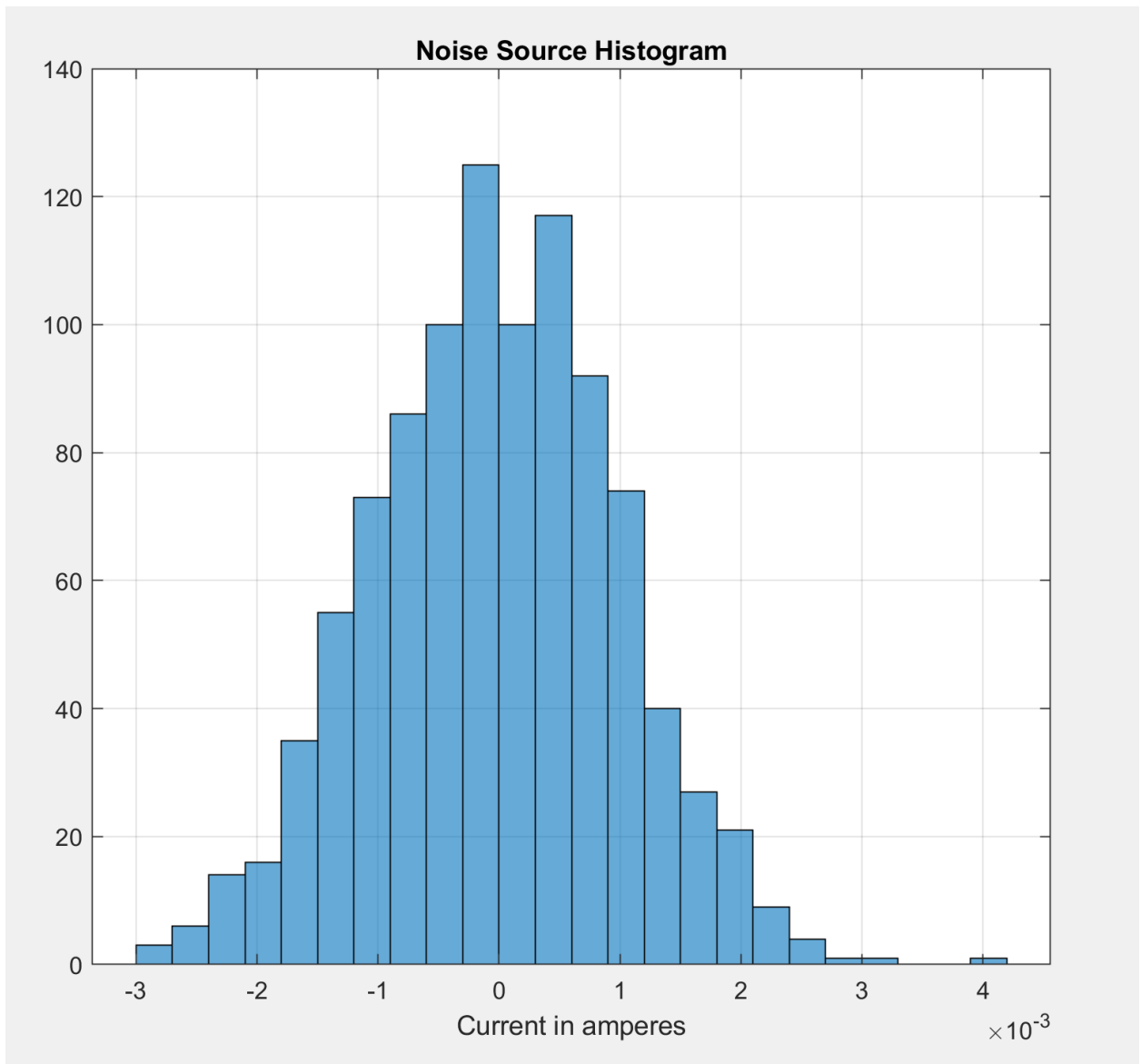


Figure 13: Noise Source Histogram

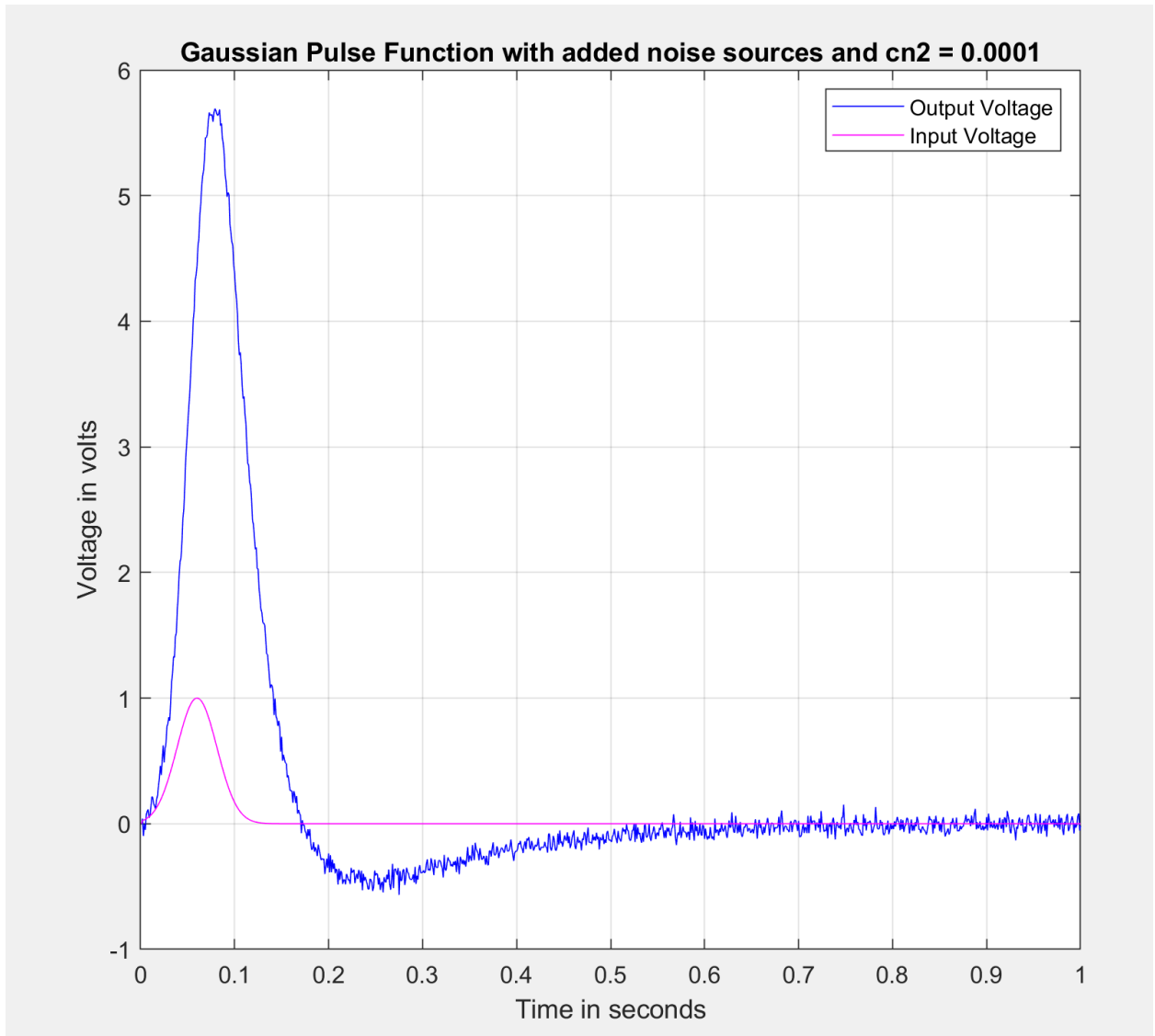


Figure 14: Gaussian Pulse function with added noise sources and $cn2=0.0001$

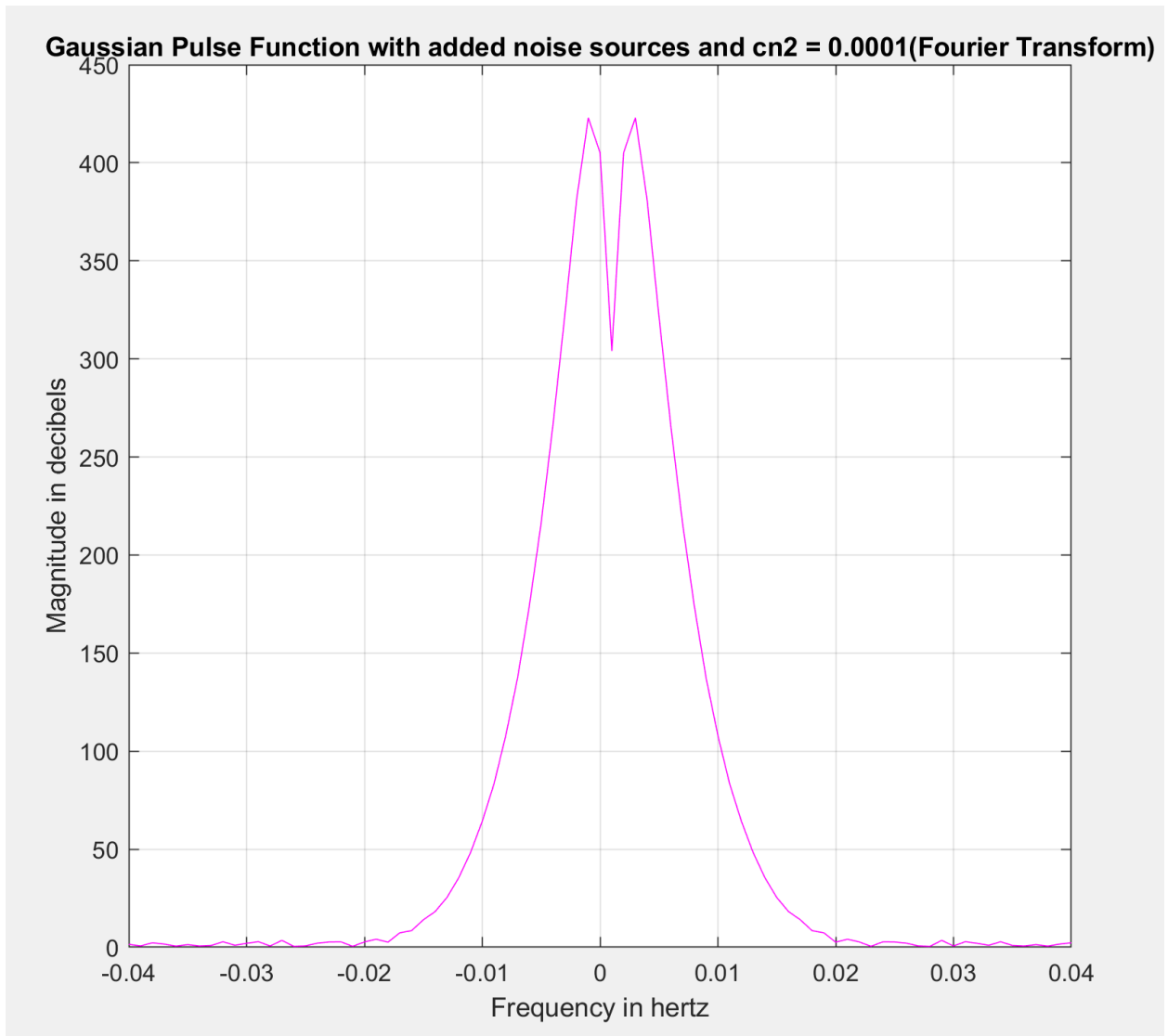


Figure 15: Gaussian Pulse Function with added noise sources and $cn2 = 0.0001$ fourier transform

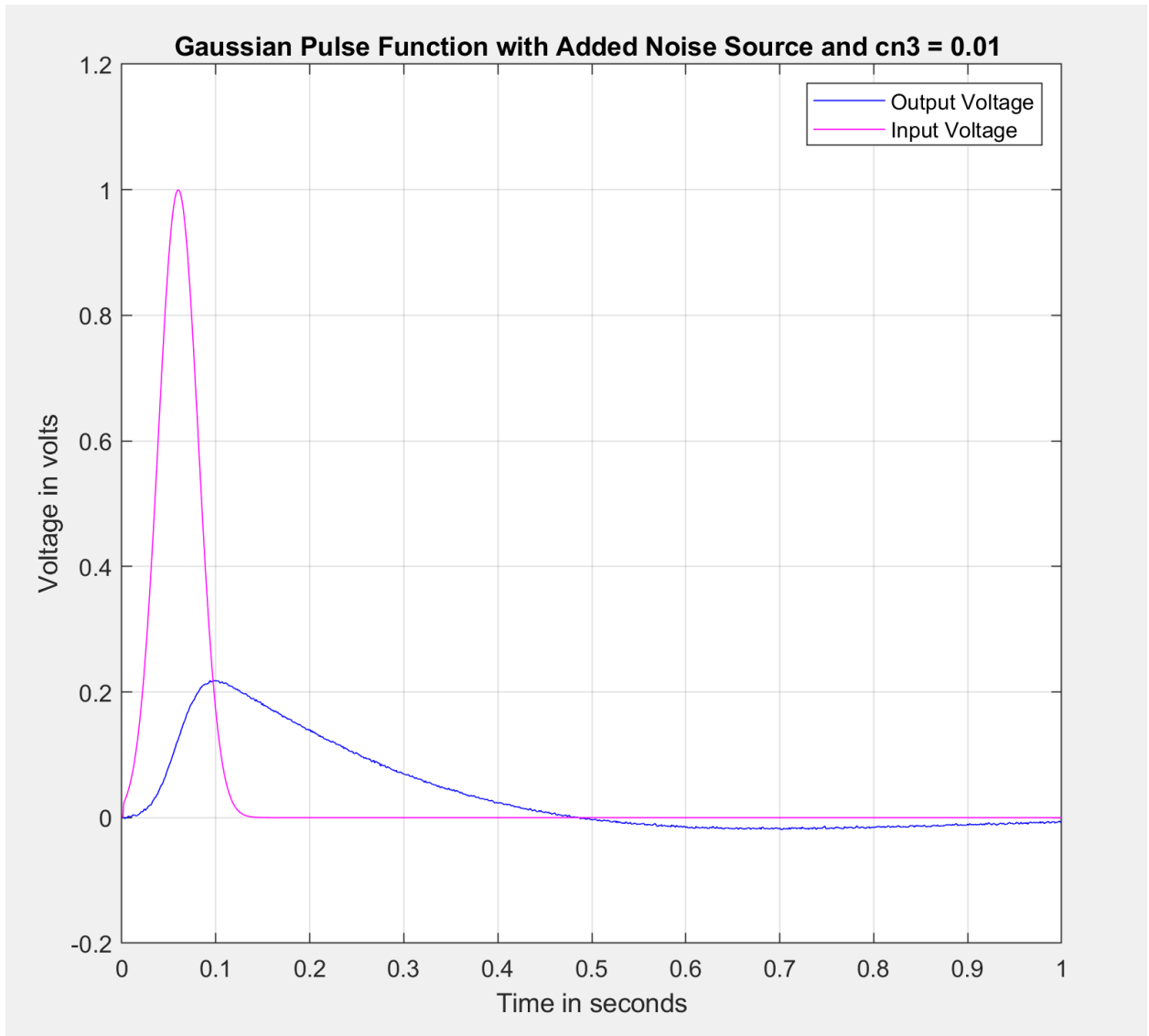


Figure 16: Gaussian Pulse function with added noise sources and $cn3=0.01$

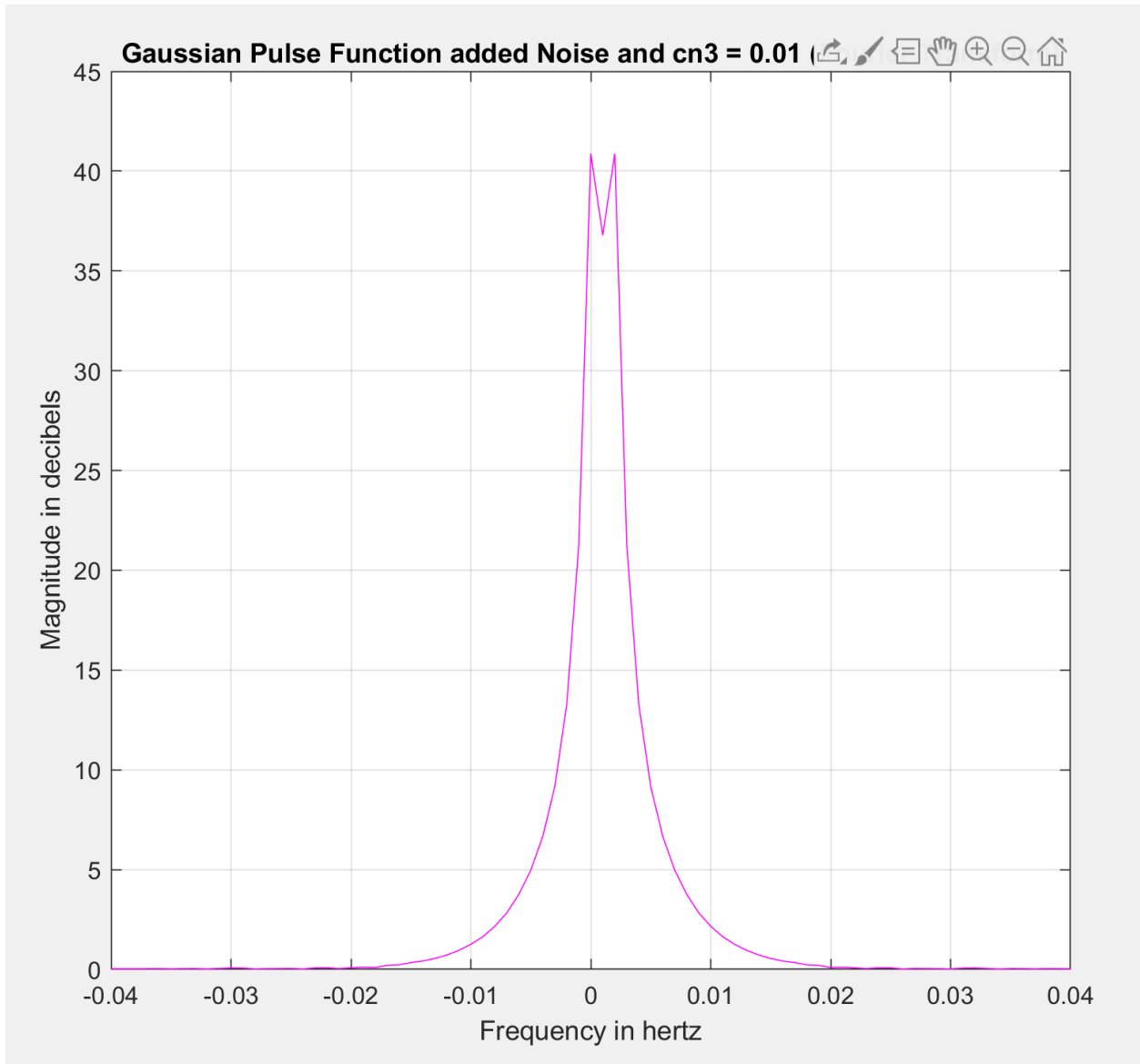


Figure 17: Gaussian Pulse function with added noise sources and $cn3=0.01$ fourier transform

We can conclude that as cn gets larger the bandwidth tends to get smaller.

Varying the timestep:

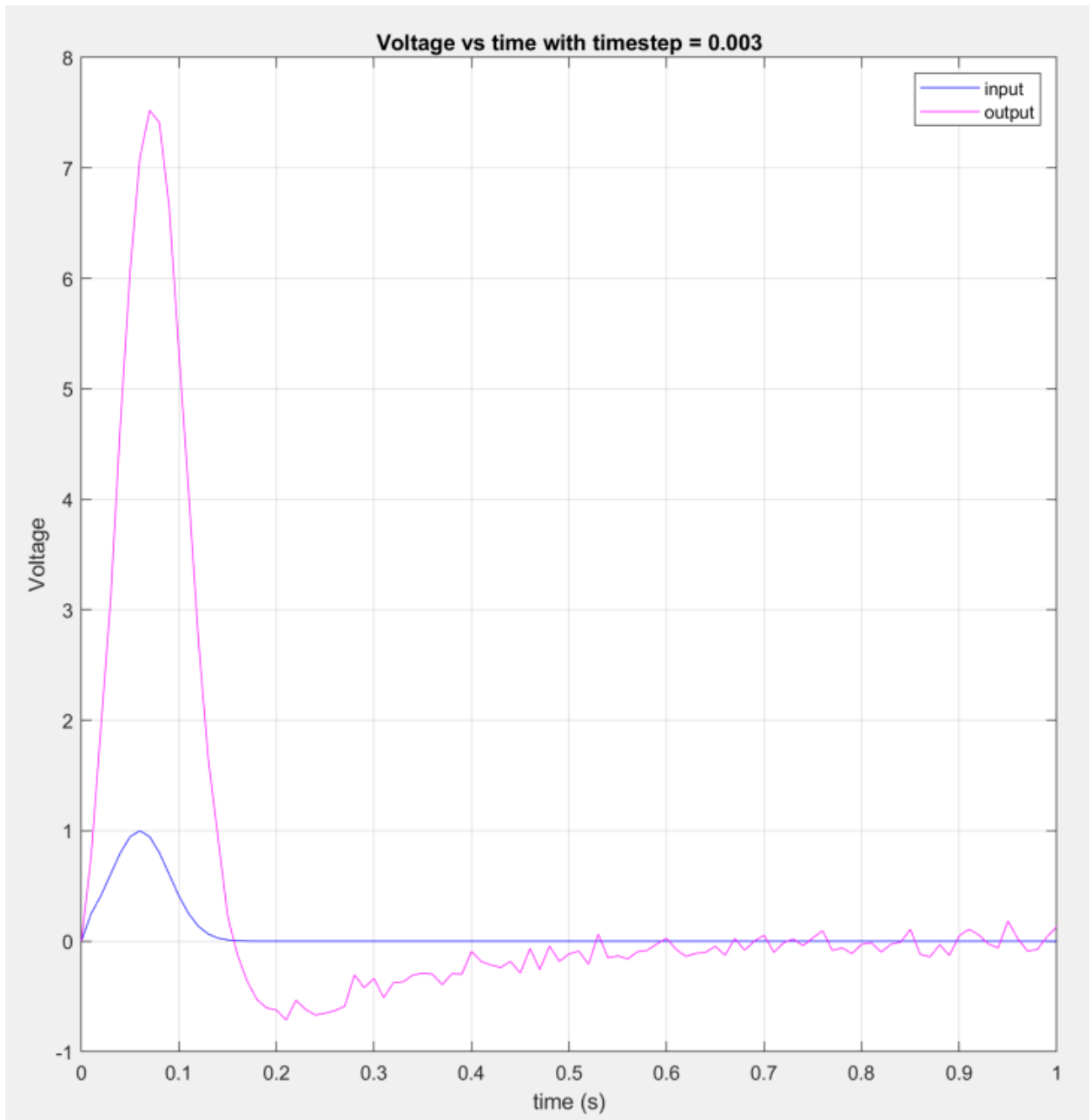


Figure 18: Plot when time step equals 0.003

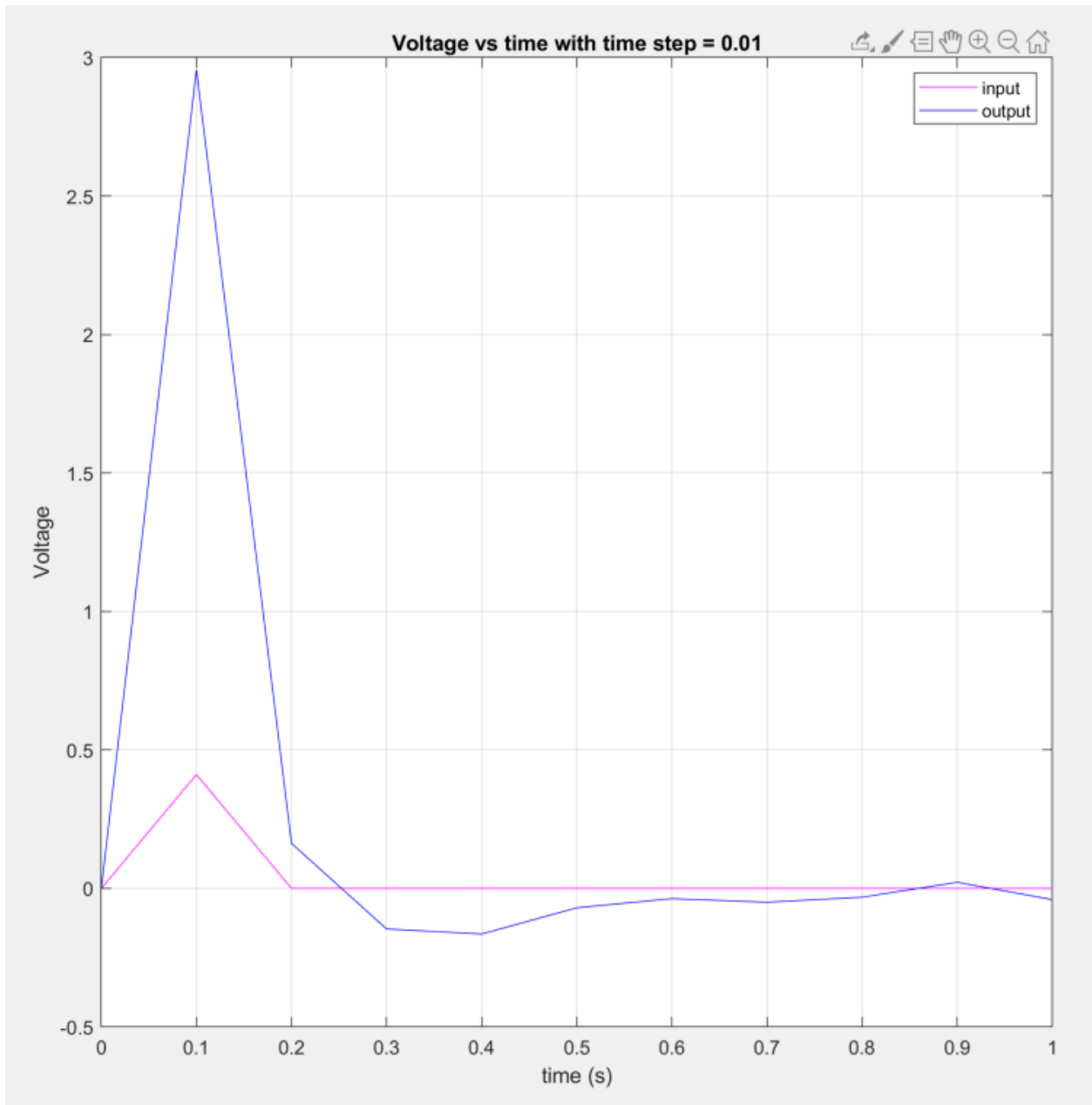


Figure19: Plot when timestep equals 0.01

What I seemed to have observed was that as the time step is increased the accuracy of the simulation decreases.

Non-Linearity:

In order to implement this in MATLAB we would need to add another matrix to represent or contain the equations for the non-linear elements. A column vector $B(V)$ would need to be added. When that has been added, because the system is

now non-linear it can't be solved by simple gaussian elimination and instead the newton Raphson numerical method would need to be used instead.

Appendix section:

```
clc
clear
clearvars
set(0,'DefaultFigureWindowSize','docked')
% Name:Jarikre Efe Jeffery
% Student Number: 101008461

%Determining the time step
voltage = linspace(0.1, 10);
current = linspace(0.1, 100);
p = polyfit(voltage, current, 1); % order 1 linear fit
fit = p(1)*voltage+p(2);
R3 = p(1);

% By taking the slope of the linear fit plot we can get the value of R3 to
% be 10.
figure(22)
plot(voltage, current, 'm.')
hold on
plot(voltage, fit)
title('Linear Fit')
grid on

clc
clear
clearvars
set(0,'DefaultFigureWindowSize','docked')
% Name:Jarikre Efe Jeffery
% Student Number: 101008461
% Part 3: Programming

G = zeros(6, 6);

%Resistances:
R1 = 1;
R2 = 2;
R3 = 10;
```



```
R4 = 0.1;  
R0 = 1000;
```

```
%Conductances:
```

```
G1 = 1/R1;  
G2 = 1/R2;  
G3 = 1/R3;  
G4 = 1/R4;  
G0 = 1/R0;
```

```
%Additional Parameters:
```

```
a = 100;  
Cval = 0.25;  
L = 0.2;  
vi = zeros(100, 1);  
vo = zeros(100, 1);  
v3 = zeros(100, 1);
```

```
G(1, 1) = 1;  
G(2, 1) = G1; G(2, 2) = -(G1 + G2); G(2, 6) = -1;  
G(3, 3) = -G3; G(3, 6) = 1;  
G(4, 3) = -a*G3; G(4, 4) = 1;  
G(5, 5) = -(G4+G0); G(5, 4) = G4;  
G(6, 2) = -1; G(6, 3) = 1;
```

```
C = zeros(6, 6);
```

```
C(2, 1) = Cval; C(2, 2) = -Cval;  
C(6, 6) = L;
```

```
F = zeros(6, 1);  
v = 0;
```

```
for vin = -10:0.1:10
```

```
    v = v + 1;  
    F(1) = vin;  
    Vm = G\F;  
    vi(v) = vin;  
    vo(v) = Vm(5);  
    v3(v) = Vm(3);
```

```
end
```

```
figure(1)
```

```

plot(vi, vo);
hold on;
plot(vi, v3);
title('VO and V3 for DC Sweep (Vin): -10 V to 10 V');
xlabel('Vin (V)')
ylabel('Vo (V)')
grid on

```

```

vo2 = zeros(1000, 1);
W = zeros(1000, 1);

```

```

Avlog = zeros(1000, 1);

```

```

for freq = linspace(0, 100, 1000)
    v = v+1;
    Vm2 = (G+1j*freq*C)\F;
    W(v) = freq;
    vo2(v) = norm(Vm2(5));

    Avlog(v) = 20*log10(norm(Vm2(5))/10);
end

```

```

figure(3)
plot(W, vo2)
hold on;
plot(W, Avlog)
grid on
title('Vo(w) dB (part C)')
xlabel('w (rad)')
ylabel('Av (dB)')

```

```

figure(4)
semilogx(W,vo2)
title('Vo(w) dB (part C)')
xlabel('w (rad)')
ylabel('Av (dB)')
grid on

```

```

w = pi;
CC = zeros(1000,1);
GG = zeros(1000,1);

```

```

for i = 1:1000

```

```

    crand = Cval + 0.05*randn();
    C(2, 1) = crand;
    C(2, 2) = -crand;
    C(3, 3) = L;
    Vm3 = (G+(1i*w*C))\F;
    CC(i) = crand;
    GG(i) = 20*log10(abs(Vm3(5))/10);
end

figure(5)
histogram(CC)
grid on
figure(6)
grid on
hist(GG)

clc
clear
clearvars
set(0,'DefaultFigureWindowStyle','docked')
% Transient simulation
R1 = 1;
R2 = 2;
C = 0.25;
L = 0.2;
R3 = 10;
a = 100;
R4 = 0.1;
R0 = 1000;
G = zeros(7,7);
Cm = zeros(7,7);
% Conductance value
G(1,1) = 1;
G(2,1) = -1/R1;
G(2,2) = 1/R1 + 1/R2;
G(2,6) = 1;
G(3,3) = 1/R3;
G(3,6) = -1;
G(4,3) = 1/R3;
G(4,7) = -1;
G(5,4) = -1/R4;
G(5,5) = 1/R4 + 1/R0;
G(6,2) = 1;
G(6,3) = -1;

```

```

G(7,4) = 1;
G(7,7) = -a;
% Capacitance value
Cm(2,1) = -C;
Cm(2,2) = C;
Cm(6,6) = -L;
V1 = zeros(7,1);
V2 = zeros(7,1);
V3 = zeros(7,1);
V_node1(1) = 0;
V_node2(1) = 0;
V_node3(1) = 0;
delta = 0.001;
A = (Cm/delta) + G;
F_index1 = zeros(7,1);
F_index2 = zeros(7,1);
F_index33 = zeros(7,1);
Vo_node1(1) = 0;
Vo_node2(1) = 0;
Vo_node3(1) = 0;

i = 1;
for j = delta:delta:1
    if j >= 0.03
        F_index1(1) = 3;
    end
    F_index2(1) = sin(2*pi*j/0.03);
    F_index33(1) = exp(-0.5*((j - 0.06)/0.03)^2);
    V1 = A\((Cm*V1/delta) + F_index1);
    V2 = A\((Cm*V2/delta) + F_index2);
    V3 = A\((Cm*V3/delta) + F_index33);
    V_node1(i+1) = V1(1);
    V_node2(i+1) = V2(1);
    V_node3(i+1) = V3(1);
    Vo_node1(i+1) = V1(5);
    Vo_node2(i+1) = V2(5);
    Vo_node3(i+1) = V3(5);
    i = i+1;
end

figure(7)
plot(0:delta:1,V_node1,'b')
hold on
plot(0:delta:1,Vo_node1,'m')

```

```

title('Voltage vs time')
xlabel('time (s)')
ylabel('Voltage')
legend('input','output')
grid on
figure(8)
plot(0:delta:1,V_node2,'b')
hold on
plot(0:delta:1,Vo_node2,'m')
title('Voltage vs time')
xlabel('time (s)')
ylabel('Voltage')
legend('input','output')
grid on
figure(9)
plot(0:delta:1,V_node3,'b')
hold on
plot(0:delta:1,Vo_node3,'m')
title('Voltage vs time')
xlabel('time (s)')
ylabel('Voltage')
legend('input','output')
grid on

```

```

% Convert to frequency domain by taking the fourier transform
step_in = fft(V_node1); %fft -> Fast fourier transform
P_mag2_in = abs(step_in/1000);
P_1_in = P_mag2_in(1:1000/2+1);
P_1_in(2:end-1) = 2*P_1_in(2:end-1);
sample_f = (1/delta)*(0:(1000/2))/1000;
% Plot figure
figure(10)
plot(sample_f,P_1_in,'b')
step_out = fft(Vo_node1);
P2_out = abs(step_out/1000);
P1_out = P2_out(1:1000/2+1);
P1_out(2:end-1) = 2*P1_out(2:end-1);
sample_f = (1/delta)*(0:(1000/2))/1000;
hold on
plot(sample_f,P1_out,'m')
title('Frequency Content Step Input')
xlabel('Frequency (Hz)')
ylabel('Amplitude')
ylim([0 3])

```

```

legend('input','output')
grid on
% The fourier transform of the step input signal gives us a sinc function.
% This makes sense as we know that by taking the fourier transform of a step signal we should
get a sinc function.
% The High Frequency components are attenuated due to the fact that the filter
% is a low pass filter

```

```

step_in = fft(V_node2); %Take fourier transform
P_mag2_in = abs(step_in/1000);
P_1_in = P_mag2_in(1:1000/2+1);
P_1_in(2:end-1) = 2*P_1_in(2:end-1); % Calculate singel ended spectrum

```

```

figure(11)
plot(sample_f,P_1_in,'b')
grid on
step_out = fft(Vo_node2);
P2_out = abs(step_out/1000);
P1_out = P2_out(1:1000/2+1);
P1_out(2:end-1) = 2*P1_out(2:end-1);
hold on
plot(sample_f,P1_out,'m')
title('Frequency Content Sinusoidal Input')
xlabel('Frequency (Hz)')
ylabel('Amplitude')
ylim([0 3])
legend('input','output')

```

```

step_in = fft(V_node3); %Take fourier transform
P_mag2_in = abs(step_in/1000);
P_1_in = P_mag2_in(1:1000/2+1);
P_1_in(2:end-1) = 2*P_1_in(2:end-1); % Calculate singel ended spectrum

```

```

figure(12)
plot(sample_f,P_1_in,'b')
grid on
step_out = fft(Vo_node3);
P2_out = abs(step_out/1000);
P1_out = P2_out(1:1000/2+1);
P1_out(2:end-1) = 2*P1_out(2:end-1);
hold on
plot(sample_f,P1_out,'m')
title('Frequency Content Gaussian Input')
xlabel('Frequency (Hz)')
ylabel('Amplitude')
ylim([0 3])
legend('input','output')

```

```
clc
clearvars
set(0,'DefaultFigureWindowStyle','docked')
```

```
R1 = 1;
R2 = 2;
R3 = 10;
R4 = 0.1;
Ro = 1000;
C = 0.25;
L = 0.2;
a = 100;
cn1 = 0.00001;
cn2 = 0.0001;
cn3 = 0.01;
```

```
C1(1,:)=[C -C 0 0 0 0 0 0];
C1(2,:)=[-C C 0 0 0 0 0 0];
C1(3,:)=[0 0 cn1 0 0 0 0 0];
C1(4,:)=[0 0 0 0 0 0 0 0];
C1(5,:)=[0 0 0 0 0 0 0 0];
C1(6,:)=[0 0 0 0 0 -L 0 0];
C1(7,:)=[0 0 0 0 0 0 0 0];
C1(8,:)=[0 0 0 0 0 0 0 0];
```

C1

```
C2(1,:)=[C -C 0 0 0 0 0 0];
C2(2,:)=[-C C 0 0 0 0 0 0];
C2(3,:)=[0 0 cn2 0 0 0 0 0];
C2(4,:)=[0 0 0 0 0 0 0 0];
C2(5,:)=[0 0 0 0 0 0 0 0];
C2(6,:)=[0 0 0 0 0 -L 0 0];
C2(7,:)=[0 0 0 0 0 0 0 0];
C2(8,:)=[0 0 0 0 0 0 0 0];
```

C2

```
C3(1,:)=[C -C 0 0 0 0 0 0];
C3(2,:)=[-C C 0 0 0 0 0 0];
C3(3,:)=[0 0 cn3 0 0 0 0 0];
C3(4,:)=[0 0 0 0 0 0 0 0];
C3(5,:)=[0 0 0 0 0 0 0 0];
```

```

C3(6,:)= [0 0 0 0 0 -L 0 0];
C3(7,:)= [0 0 0 0 0 0 0 0];
C3(8,:)= [0 0 0 0 0 0 0 0];

```

C3

```

G(1,:)= [1 -1 0 0 0 0 0 1];
G(2,:)= [-1 1.5 0 0 0 1 0 0];
G(3,:)= [0 0 0.1 0 0 -1 0 0];
G(4,:)= [0 0 0 10 -10 0 1 0];
G(5,:)= [0 0 0 -10 10.0010 0 0 0];
G(6,:)= [0 1 -1 0 0 -L 0 0];
G(7,:)= [0 0 -10 1 0 0 0 0];
G(8,:)= [1 0 0 0 0 0 0 0];

```

G

```

F = [
    0 ;
    0 ;
    0 ;
    0 ;
    0 ;
    0 ;
    0 ;
    0 ;
    0 ;
    ];

```

% Given these values from lab manual

```

delta = 0.001;
standard_deviation = 0.03;
d = 0.06;
m = 1;
c_s = zeros(1,1000);
f_l = zeros(8,1,1000);

```

```

for i=1:1:1000
    f_l(8,1,i) = exp(-((i*delta - d)/standard_deviation)^2);
    f_l(3,1,i) = -0.001*randn;
    c_s(i) = f_l(3,1,i);
end

```

```

VL_1 = zeros(8,1,1000);
VL_2 = zeros(8,1,1000);

```



```
VL_3 = zeros(8,1,1000);
```

```
for i = 2:1:1000
    index1 = C1/delta + G;
    index2 = C2/delta + G;
    index3 = C3/delta + G;

    VL_1(:,i) = index1\((C1*VL_1(:,i-1))/delta + f_l(:,i));
    VL_2(:,i) = index2\((C1*VL_2(:,i-1))/delta + f_l(:,i));
    VL_3(:,i) = index3\((C1*VL_3(:,i-1))/delta + f_l(:,i));
end
```

```
VoL_1(1,:) = VL_1(5,1,:);
ViL_1(1,:) = VL_1(1,1,:);
```

```
VoL_2(1,:) = VL_2(5,1,:);
ViL_2(1,:) = VL_2(1,1,:);
```

```
VoL_3(1,:) = VL_3(5,1,:);
ViL_3(1,:) = VL_3(1,1,:);
```

```
figure(13)
plot((1:1000).*delta, VoL_1(1,:), 'b')
hold on
plot((1:1000).*delta, ViL_1(1,:), 'm')
title('Gaussian Pulse Function with added noise sources and cn1 = 0.00001')
xlabel('Time (s)')
ylabel('Voltage (v)')
grid on
legend('Output Voltage', 'Input Voltage')
hold off
```

```
figure(14)
histogram(c_s)
title('Noise Source Histogram')
grid on
xlabel('Current in amperes')
```

```
figure(15)
FF = abs(fftshift(fft(VoL_1(1,:))));
plot(((1:length(FF))/1000)-0.5, FF, 'b')
xlabel('Frequency in hertz')
```

```

ylabel('Magnitude in decibels')
grid on
xlim([-0.04 0.04])
title('Gaussian Pulse Function with added noise sources and cn1 = 0.00001(Fourier Transform)')

```

```

% CN 2 -----

```

```

figure(16)
plot((1:1000).*delta, VoL_2(1,:), 'b')
hold on
plot((1:1000).*delta, ViL_2(1,:), 'm')
title('Gaussian Pulse Function with added noise sources and cn2 = 0.0001')
xlabel('Time in seconds')
ylabel('Voltage in volts')
grid on
legend('Output Voltage', 'Input Voltage')
hold off

```

```

figure(17)
FF = abs(fftshift(fft(VoL_2(1,:)))));
plot(((1:length(FF))/1000)-0.5, FF, 'm')
xlabel('Frequency in hertz')
ylabel('Magnitude in decibels')
grid on
xlim([-0.04 0.04])
title('Gaussian Pulse Function with added noise sources and cn2 = 0.0001(Fourier Transform)')

```

```

figure(18)
plot((1:1000).*delta, VoL_3(1,:), 'b')
hold on
plot((1:1000).*delta, ViL_3(1,:), 'm')
title('Gaussian Pulse Function with Added Noise Source and cn3 = 0.01 ')
xlabel('Time in seconds')
ylabel('Voltage in volts')
grid on
legend('Output Voltage', 'Input Voltage')
hold off

```

```

figure(19)
FF = abs(fftshift(fft(VoL_3(1,:)))));
plot(((1:length(FF))/1000)-0.5, FF, 'm')
xlabel('Frequency in hertz')
ylabel('Magnitude in decibels')
grid on

```

```

xlim([-0.04 0.04])
title('Gaussian Pulse Function added Noise and cn3 = 0.01 (Fourier Transform)')
% Varying timestep
%Varying timestep:
clc
clear
clearvars
set(0,'DefaultFigureWindowStyle','docked')
R1 = 1;
R2 = 2;
C = 0.25;
L = 0.2;
R3 = 10;
a = 100;
R4 = 0.1;
R0 = 1000;

G = zeros(7,7);
C_mat = zeros(7,7);
G(1,1) = 1;
G(2,1) = -1/R1;
G(2,2) = 1/R1 + 1/R2;
G(2,6) = 1;
G(3,3) = 1/R3;
G(3,6) = -1;
G(4,3) = 1/R3;
G(4,7) = -1;
G(5,4) = -1/R4;
G(5,5) = 1/R4 + 1/R0;
G(6,2) = 1;
G(6,3) = -1;
G(7,4) = 1;
G(7,7) = -a;
C_mat(2,1) = -C;
C_mat(2,2) = C;
C_mat(6,6) = -L;

G
C_mat

F = zeros(7,1);
V = zeros(7,1);

%Circuit with noise

```

```
In = 0.001; % as provided in assignment manual
Cn = 0.00001; % as provided in assignment manual
C_mat(3,3) = Cn;
G
C_mat
```

```
delta = 0.001;
A_transpse = C_mat/delta + G;
```

```
F = zeros(7,1);
V = zeros(7,1);
Vo_index(1) = 0;
Vi_index(1) = 0;
```

```
ii = 1;
for t = delta:delta:1
    F(1) = exp(-0.5*((t - 0.06)/0.03)^2);
    F(3) = In*normrnd(0,1);
    V = A_transpse\'(C_mat*V/delta + F);
    Vi_index(ii + 1) = F(1);
    Vo_index(ii + 1) = V(5);
    ii = ii + 1;
end
```

```
X_input = fft(Vi_index);
P2_input = abs(X_input/1000);
P1_input = P2_input(1:1000/2+1);
P1_input(2:end-1) = 2*P1_input(2:end-1);
f = (1/delta)*(0:(1000/2))/1000;
```

```
X_output = fft(Vo_index);
P2_output = abs(X_output/1000);
P1_output = P2_output(1:1000/2+1);
P1_output(2:end-1) = 2*P1_output(2:end-1);
f = (1/delta)*(0:(1000/2))/1000;
```

```
C_sml = C_mat;
C_med = C_mat;
C_big = C_mat;
C_sml(3,3) = 0;
C_med(3,3) = 0.001;
C_big(3,3) = 0.1;
V_sml = zeros(7,1);
V_med = zeros(7,1);
```

```

V_big = zeros(7,1);
Vo_sml(1) = 0;
Voutput_med(1) = 0;
Vout_big(1) = 0;
Vi_index(1) = 0;
ii = 1;
for t = delta:delta:1
    F(1) = exp(-0.5*((t - 0.06)/0.03)^2);
    F(3) = ln*normrnd(0,1);
    V_sml = (C_sml/delta + G)\(C_sml*V_sml/delta + F);
    V_med = (C_med/delta + G)\(C_med*V_med/delta + F);
    V_big = (C_big/delta + G)\(C_big*V_big/delta + F);
    Vo_sml(ii + 1) = V_sml(5);
    Voutput_med(ii + 1) = V_med(5);
    Vout_big(ii + 1) = V_big(5);
    Vi_index(ii + 1) = F(1);
    ii = ii + 1;
end

```

```

delta1 = 0.01;
Vinput_SmlStep(1) = 0;
Voutput_SmlStep(1) = 0;
V = zeros(7,1);
ii = 1;
for t = delta1:delta1:1
    F(1) = exp(-0.5*((t - 0.06)/0.03)^2);
    F(3) = ln*normrnd(0,1);
    V = (C_mat/delta1 + G)\(C_mat*V/delta1 + F);
    Voutput_SmlStep(ii + 1) = V(5);
    Vinput_SmlStep(ii + 1) = F(1);
    ii = ii + 1;
end

```

```

delta2 = 0.1;
Vinput_bigStep(1) = 0;
Voutput_bigStep(1) = 0;
V = zeros(7,1);
ii = 1;
for t = delta2:delta2:1
    F(1) = exp(-0.5*((t - 0.06)/0.03)^2);
    F(3) = ln*normrnd(0,1);
    V = (C_mat/delta2 + G)\(C_mat*V/delta2 + F);
    Voutput_bigStep(ii + 1) = V(5);
    Vinput_bigStep(ii + 1) = F(1);
end

```

```
    ii = ii + 1;  
end
```

```
figure(20)  
plot(0:delta1:1,Vinput_SmlStep,'b')  
hold on  
plot(0:delta1:1,Voutput_SmlStep,'m')  
title('Voltage vs time with timestep = 0.003')  
xlabel('time (s)')  
ylabel('Voltage')  
legend('input','output')  
grid on
```

```
figure(21)  
plot(0:delta2:1,Vinput_bigStep,'m')  
hold on  
plot(0:delta2:1,Voutput_bigStep,'b')  
title('Voltage vs time with time step = 0.01')  
xlabel('time (s)')  
ylabel('Voltage')  
legend('input','output')  
grid on
```